

Processor Logic Design

Lesson-11:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Processor organization	<ul style="list-style-type: none">• To understand the bus organization, memory organization, etc.• To know the importance of scratchpad memory and accumulator register.• Compare different processor organization	Class Lecture Question and answer	Test, exams, quiz, etc

Introduction

□ Terminologies


- Processor unit (Datapath)
 - Processes digital data
- Control Unit
 - Specifies the operation to be performed by processor
- CPU
 - Combination of processor and control unit
- ALU
 - A combinational circuit which is able to perform arithmetic and logical operations.

Processor Organization

□ Bus Organization

Perform

$$R1 \leftarrow R2 + R3$$

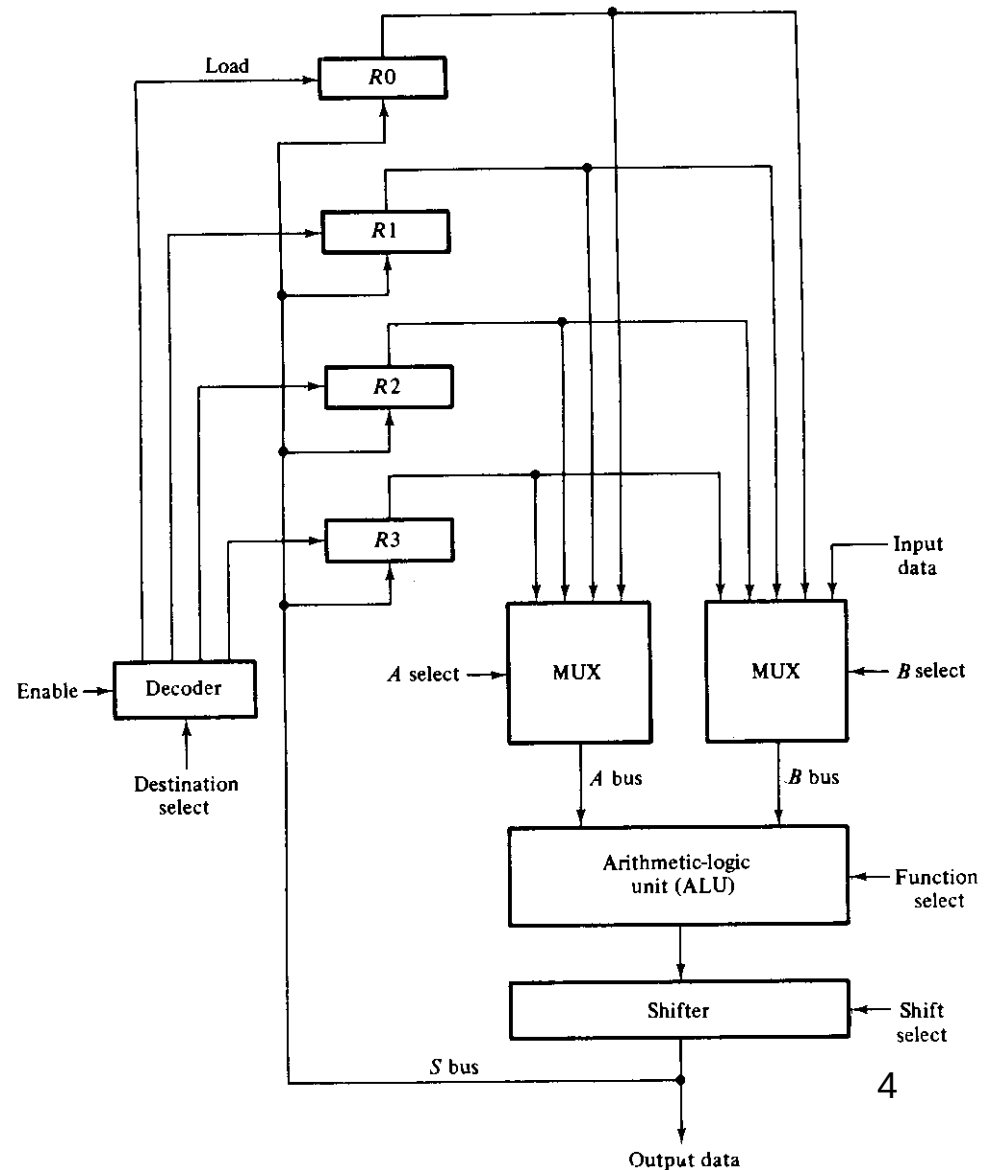

Processor Organization

❑ Scratchpad memory


- Alternative to many registers a single memory unit can be used
- Such memory unit is called scratchpad memory.
- It is different from the main memory.
- Figure shows a processor with scratchpad memory

Processor Organization

❑ Scratchpad memory

Perform

$R1 \leftarrow R2 + R3$

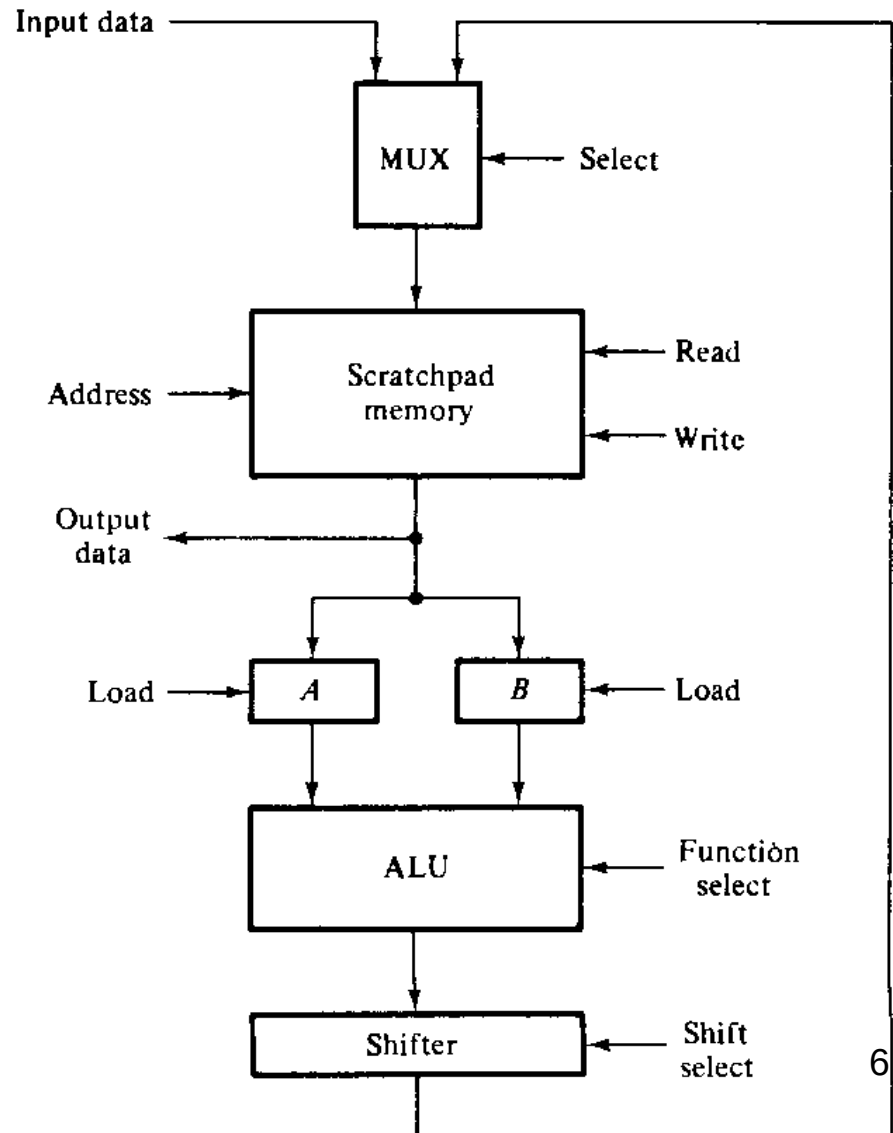


Processor Organization

□ Two-port Scratchpad memory

Perform

$$R1 \leftarrow R2 + R3$$

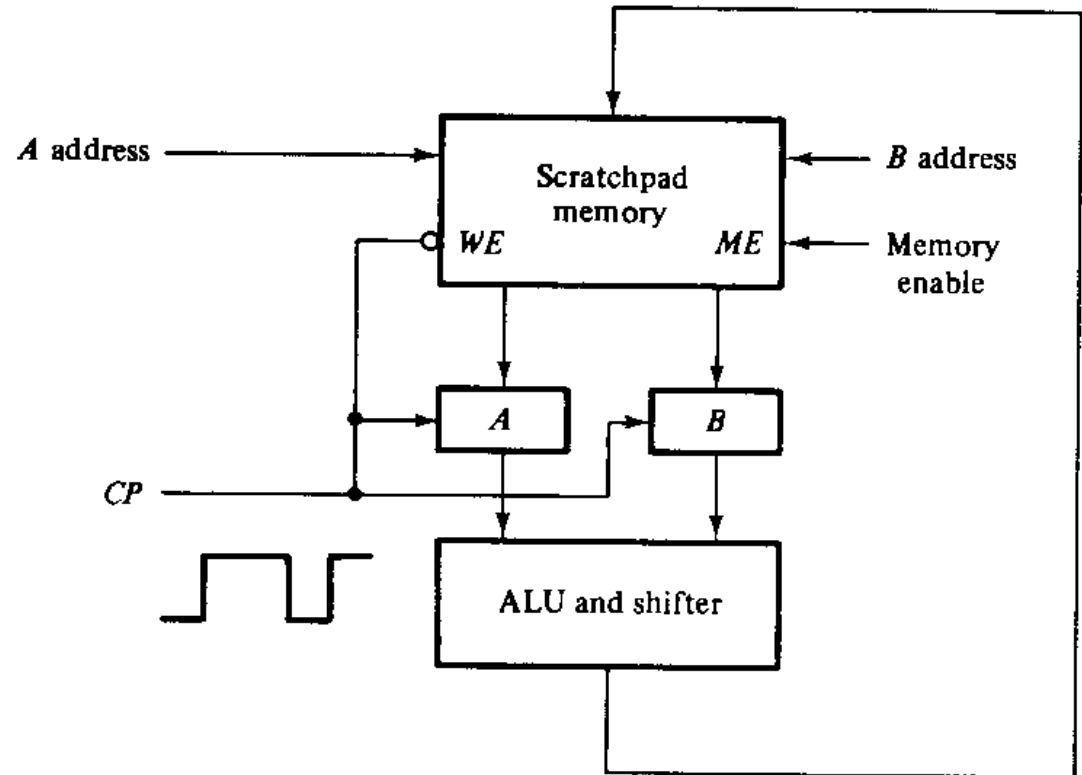


Processor Organization

❑ Accumulator Register

- Different from other memory registers
- Used to perform serial addition

Perform

$R1 \leftarrow R2 + R3$

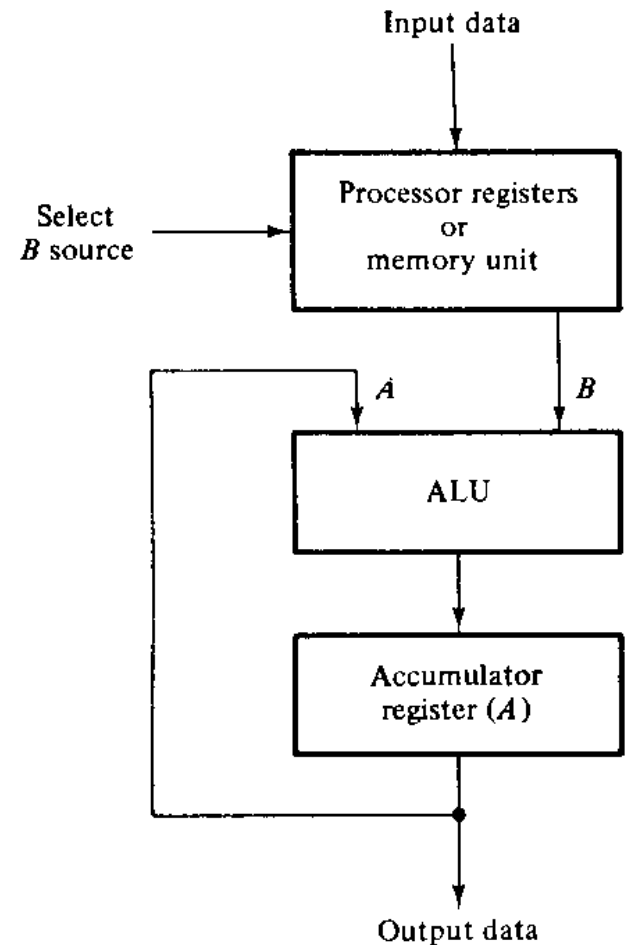


Processor Organization

- Generic Datapath

Perform

$$R1 \leftarrow R2 + R3$$

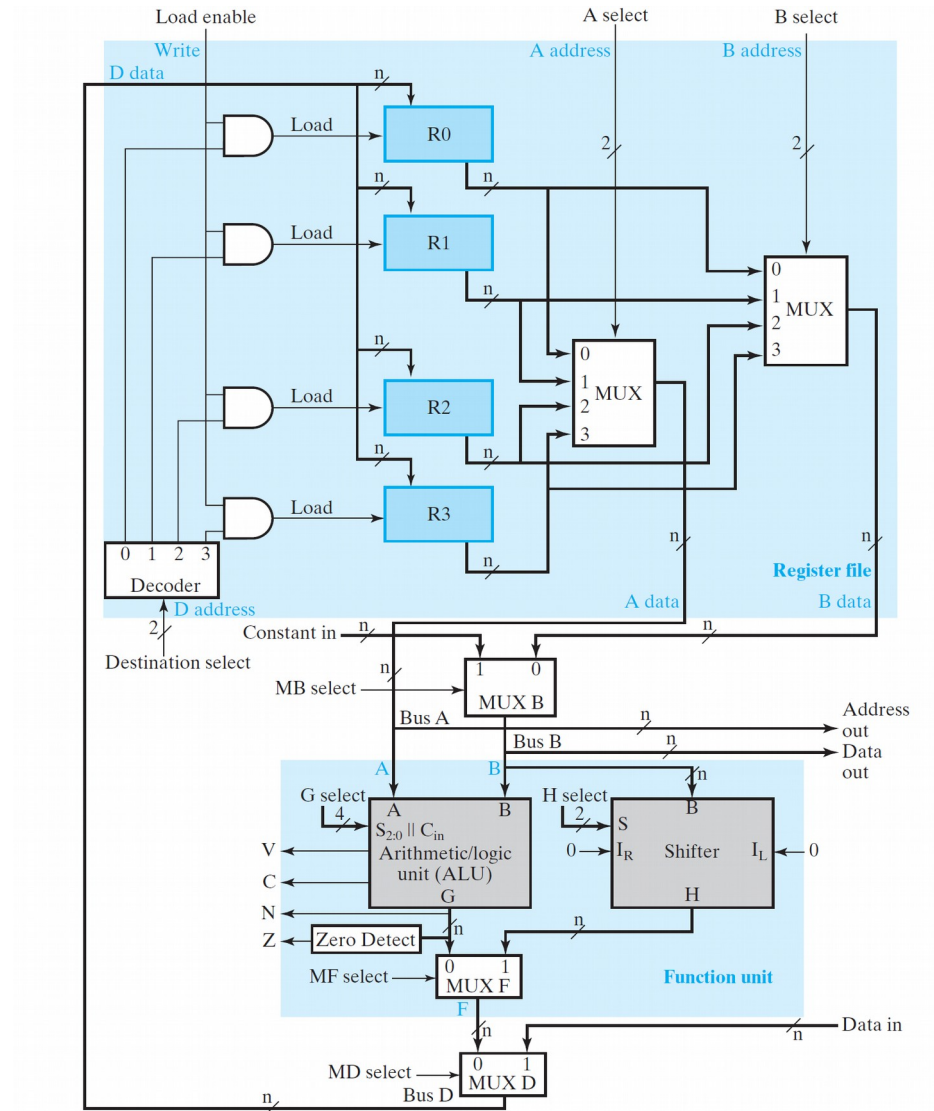


Lesson-12:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Arithmetic unit	<ul style="list-style-type: none">• To understand the design principles of arithmetic unit• To design arithmetic unit with a given set of arithmetic operations.	Class Lecture PBL (Solving some problems in class)	Test, exams, quiz, etc

Arithmetic Logic Unit

□ The ALU

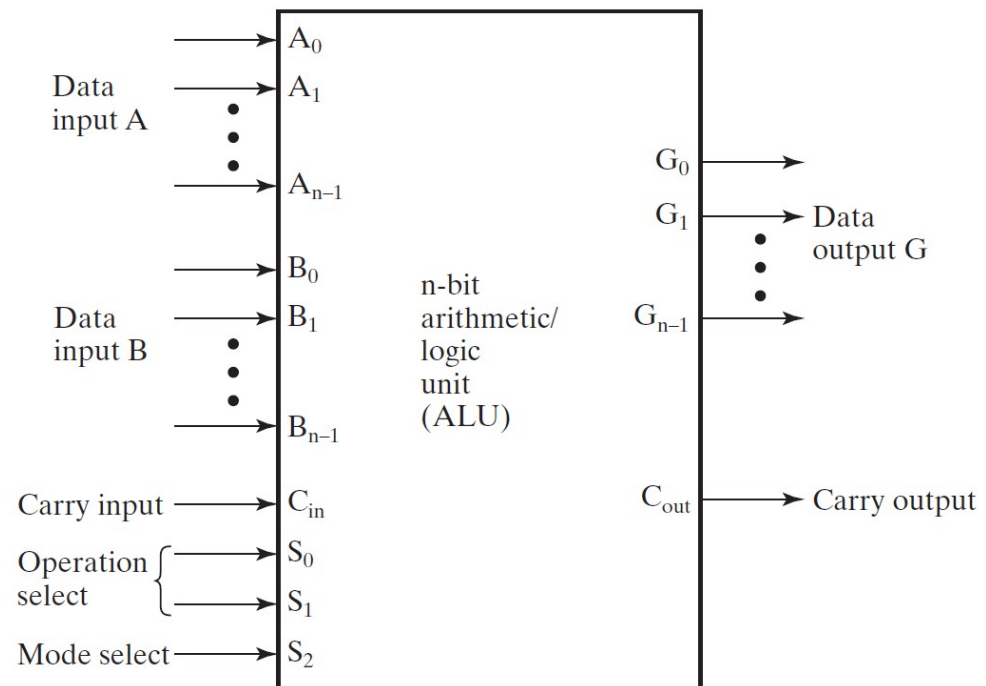
- Multi-operational Combinational Circuit.
- Fig. Shows a n-bit ALU
- Design Steeps
 - **Design of Arithmetic Unit.**
 - **Design of Logic Unit**
 - **Combine the above two.**



Arithmetic Logic Unit

□ Design of Arithmetic Unit

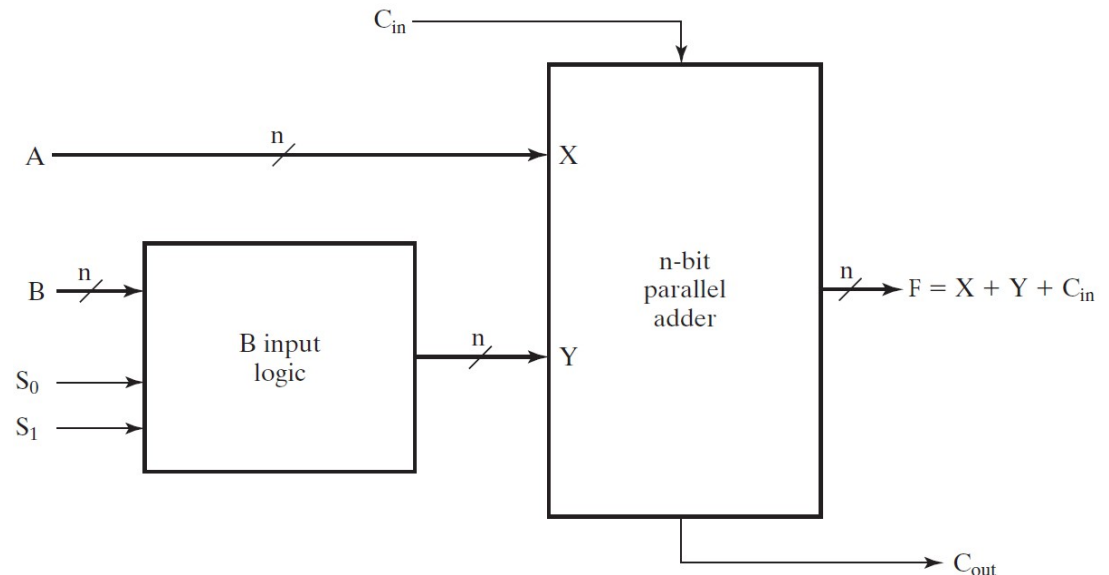- Basic component is a parallel-adder.
- Fig. shows a n-bit arithmetic circuit
- Basic operations to be performed by the full-adder
 - **Addition**
 - **Subtraction**
 - **Increment**
 - **Decrement**
 - **Transfer**











Arithmetic Logic Unit

□ Parallel-adder

- Operations performed by changing only one variable of PA

Select		Input	$F = (A + Y + C_{in})$	
S_1	S_0	Y	$C_{in} = 0$	$C_{in} = 1$
0	0	all 0s	$G = A$ (transfer)	$G = A + 1$ (increment)
0	1	B	$G = A + B$ (add)	$G = A + B + 1$
1	0	\bar{B}	$G = A + \bar{B}$	$G = A + \bar{B} + 1$ (subtract)
1	1	all 1s	$G = A - 1$ (decrement)	$G = A$ (transfer)

        


Arithmetic Logic Unit

□ Design of Arithmetic Unit


- To combine all these operations we need 2 selection variables along with carry.
- **Note that the operations can be performed only by changing the B input and the carry.**
- **The selection circuit**

Inputs			Output
S_1	S_0	B_i	Y_i
0	0	0	0 $Y_i = 0$
0	0	1	0
0	1	0	0 $Y_i = B_i$
0	1	1	1
1	0	0	1 $Y_i = \overline{B_i}$
1	0	1	0
1	1	0	1 $Y_i = 1$
1	1	1	1

(a) Truth table

 

 (b) Map simplification:
 $Y_i = B_i S_0 + \overline{B_i} S_1$



s_1	s_0	Y_i
0	0	0
0	1	B_i
1	0	B_i'
1	1	1


Arithmetic Logic Unit

□ Design of Arithmetic Unit

– The logic diagram

$$X_i = A_i$$
 
$$Y_i = B_i s_0 + B'_i s_1 \quad i = 1, 2, \dots, n$$



Function select			Y equals	Output equals	Function
s_1	s_0	C_{in}			
0	0	0	0	$F = A$	Transfer A
0	0	1	0	$F = A + 1$	Increment A
0	1	0	B	$F = A + B$	Add B to A
0	1	1	B	$F = A + B + 1$	Add B to A plus 1
1	0	0	\bar{B}	$F = A + \bar{B}$	Add 1's complement of B to A
1	0	1	\bar{B}	$F = A + \bar{B} + 1$	Add 2's complement of B to A
1	1	0	All 1's	$F = A - 1$	Decrement A
1	1	1	All 1's	$F = A$	Transfer A

Arithmetic Logic Unit


□ Design other arithmetic circuit

- **Example:** Design an arithmetic circuit with
 - When $s=0$ perform $A+B$
 - When $s=1$ perform $A-B$
- **Solution**
 - $A+B$ requires
 - $C_{in}=0$, $X_i=A_i$ and $Y_i=B_i$
 - $A-B$ requires
 - $C_{in}=1$, $X_i=A_i$ and $Y_i=B_i'$

Arithmetic Logic Unit

□ Design other arithmetic circuit

S=0 : Perform A+B
S=1 : Perform A-B

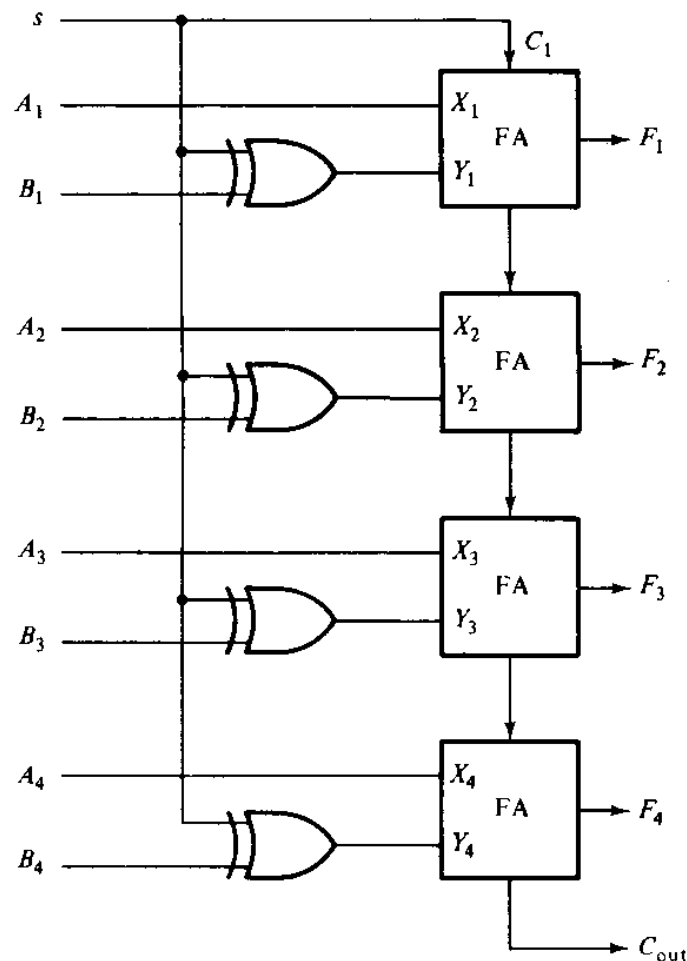


Lesson-13:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Logical Unit and ALU	<ul style="list-style-type: none">• To design of logical unit• To design ALU by combining arithmetic and logic unit.	Class Lecture PBL (Solving some problems in class)	Test, exams, quiz, etc

Arithmetic Logic Unit

□ Design of Logic Unit

 


(a) Logic diagram

s_1	s_0	Output	Operation
0	0	$F_i = A_i + B_i$	OR
0	1	$F_i = A_i \oplus B_i$	XOR
1	0	$F_i = A_i B_i$	AND
1	1	$F_i = A_i'$	NOT

(b) Function table

Arithmetic Logic Unit

Combining Arithmetic and Logic Unit

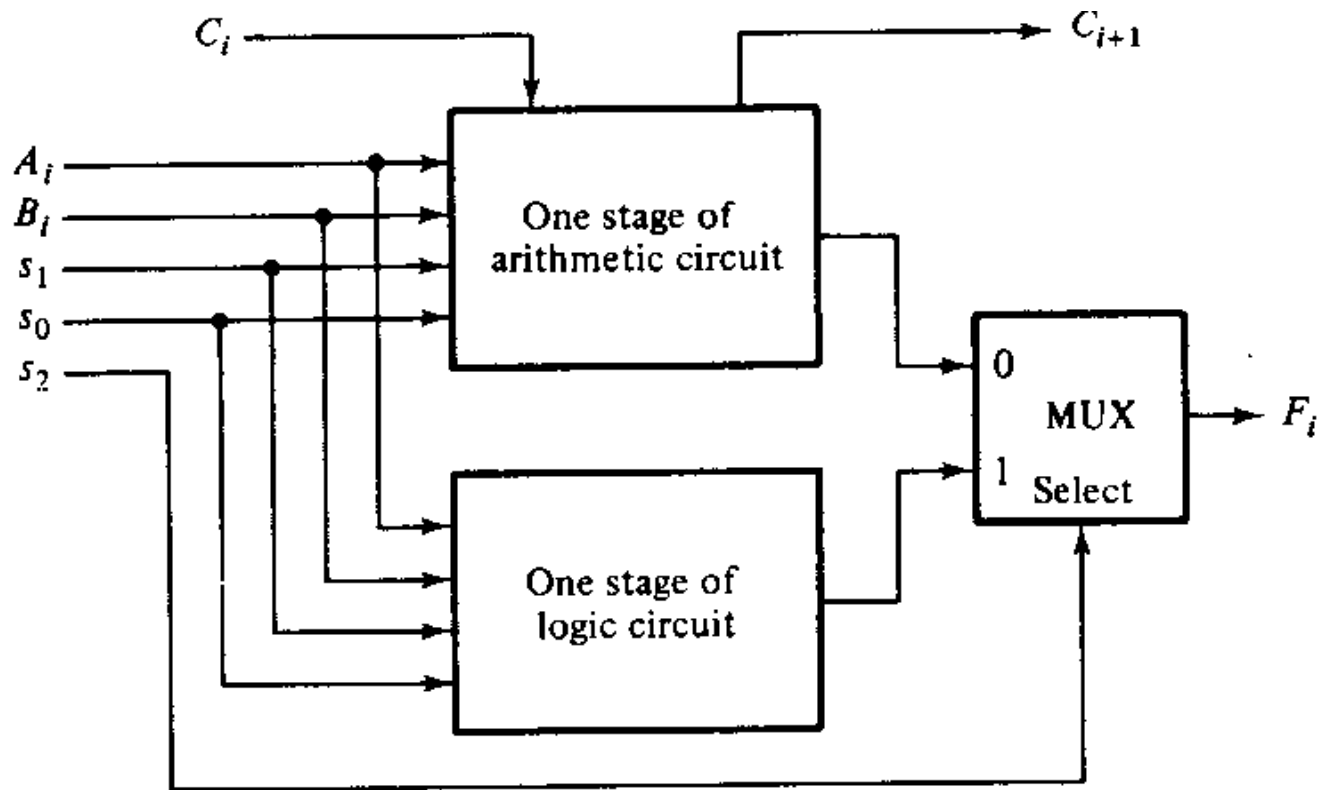

Arithmetic Logic Unit

□ How to Design More Efficient ALU

- Note
 - Full-adder with $C_{in}=0$ performs XOR
 - Table lists the possible operations

s_2	s_1	s_0	X_i	Y_i	C_i	$F_i = X_i \oplus Y_i$	Operation	Required operation
1	0	0	A_i	0	0	$F_i = A_i$	Transfer A	OR
1	0	1	A_i	B_i	0	$F_i = A_i \oplus B_i$	XOR	XOR
1	1	0	A_i	B_i'	0	$F_i = A_i \odot B_i$	Equivalence	AND
1	1	1	A_i	1	0	$F_i = A_i'$	NOT	NOT

- Therefore, more efficient ALU design may be possible

Arithmetic Logic Unit

- More Efficient ALU

- With $s_2s_1s_0=100$

- $Y_i=0$, hence we need to change X_i from A_i to A_i+B_i

- With $s_2s_1s_0=110$

- Lets make a similarity with previous case
- Change X_i from A_i to A_i+K_i

$$F_i = X_i \oplus Y_i = (A_i + K_i) \oplus B'_i = A_i B_i + K_i B_i + A'_i K'_i B'_i$$

- Consider $K_i = B'_i$

$$F_i = A_i B_i + B'_i B_i + A_i B_i B'_i = A_i B_i$$

s_2	s_1	s_0	X_i	Y_i	C_i	$F_i = X_i \oplus Y_i$	Operation	Required operation
1	0	0	A_i	0	0	$F_i = A_i$	Transfer A	OR
1	0	1	A_i	B_i	0	$F_i = A_i \oplus B_i$	XOR	XOR
1	1	0	A_i	B'_i	0	$F_i = A_i \odot B_i$	Equivalence	AND
1	1	1	A_i	1	0	$F_i = A'_i$	NOT	NOT

Arithmetic Logic Unit

- More Efficient ALU

- Finally the inputs of the full adders are

$$X_i = A_i + s_2 s'_1 s'_0 B_i + s_2 s_1 s'_0 B'_i$$

$$Y_i = s_0 B_i + s_1 B'_i$$

$$Z_i = s'_2 C_i$$

- If $s_2=0$


$$X_i = A_i$$

$$Y_i = s_0 B_i + s_1 B'_i$$

$$Z_i = C_i$$

Arithmetic Logic Unit

More Efficient ALU

 


Lesson-14:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Status register and shifter in ALU	<ul style="list-style-type: none">• To understand the design principle of Complete ALU and its components• To know the importance and use of status register in ALU.• To design shift register by using combinational circuit.	Class Lecture PBL (Solving some problems in class)	Test, exams, quiz, etc

Arithmetic Logic Unit

□ Status Register

 

Arithmetic Logic Unit

□ Status bits after subtraction of two unsigned numbers (**A-B**)

Relation	Condition of status bits	Boolean function
$A > B$	$C = 1$ and $Z = 0$	CZ'
$A \geq B$	$C = 1$	C
$A < B$	$C = 0$	C'
$A \leq B$	$C = 0$ or $Z = 1$	$C' + Z$
$A = B$	$Z = 1$	Z
$A \neq B$	$Z = 0$	Z'


Design of Shifter

□ The Shift Unit

- Connected after ALU.
 - **Bidirectional Shift register with parallel load can be used.**
 - **But it requires 3 clock-pulses**
 - **A combination circuit that can perform shift operation is a good choice**
 - **Requires only one clock-puls.**

Design of Shifter

□ Combinational Shift Unit

 

Design of Shifter


□ Function table of the shifter

H_1	H_0	Operation	Function
0	0	$S \leftarrow F$	Transfer F to S (no shift)
0	1	$S \leftarrow \text{shr } F$	Shift-right F into S
1	0	$S \leftarrow \text{shl } F$	Shift-left F into S
1	1	$S \leftarrow 0$	Transfer 0's into S

Design of Shifter

□ Barrel shifter

 - Often the data must be shifted more than one bit position in a single clock cycle.
- A *barrel shifter* is designed to do this as shown in Fig.




Lesson-15:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Processor Unit	<ul style="list-style-type: none">• To construct a processor unit by using the designed ALU• To understand the control word of processor and how they can use to perform various microoperations	Class Lecture Question and answer	Test, exams, quiz, etc


Processor Unit

Block Diagram

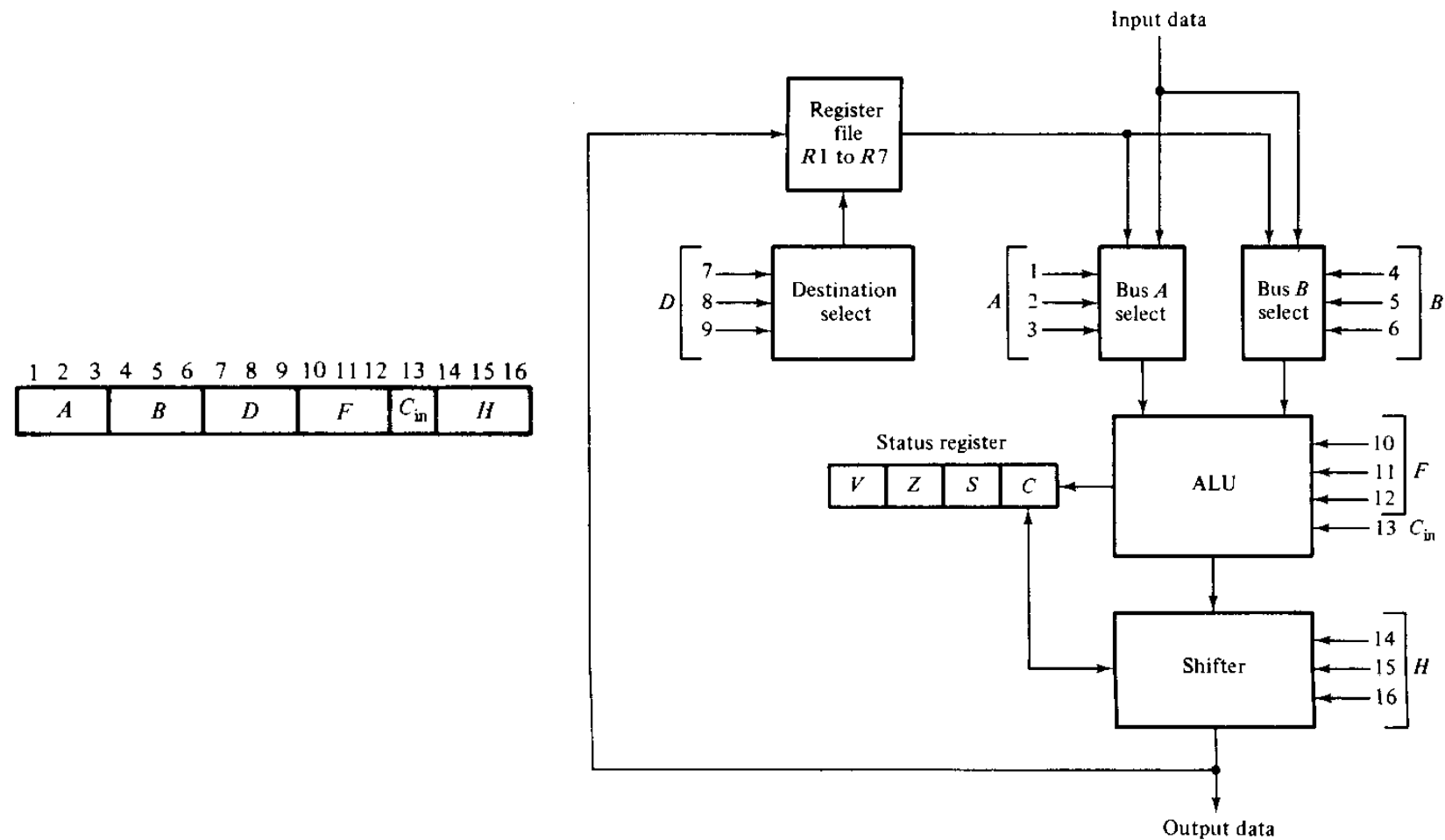

Processor Unit

Block Diagram with functions

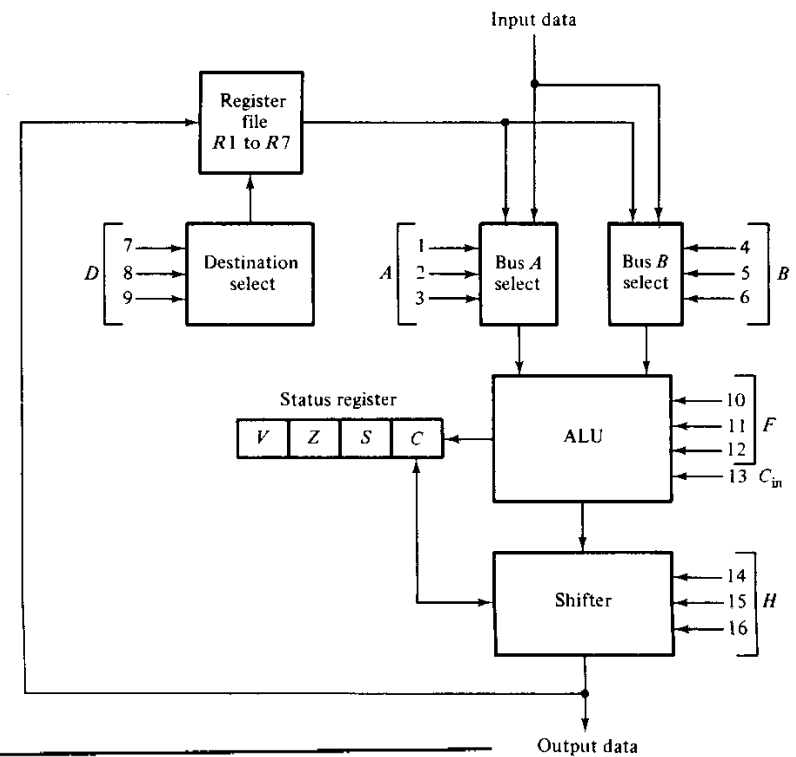

Binary code	Function of selection variables					
	<i>A</i>	<i>B</i>	<i>D</i>	<i>F</i> with $C_{in} = 0$	<i>F</i> with $C_{in} = 1$	<i>H</i>
0 0 0	Input data	Input data	None	$A, C \leftarrow 0$	$A + 1$	No shift
0 0 1	<i>R1</i>	<i>R1</i>	<i>R1</i>	$A + B$	$A + B + 1$	Shift-right, $I_R = 0$
0 1 0	<i>R2</i>	<i>R2</i>	<i>R2</i>	$A - B - 1$	$A - B$	Shift-left, $I_L = 0$
0 1 1	<i>R3</i>	<i>R3</i>	<i>R3</i>	$A - 1$	$A, C \leftarrow 1$	0's to output bus
1 0 0	<i>R4</i>	<i>R4</i>	<i>R4</i>	$A \vee B$	—	—
1 0 1	<i>R5</i>	<i>R5</i>	<i>R5</i>	$A \oplus B$	—	Circulate-right with <i>C</i>
1 1 0	<i>R6</i>	<i>R6</i>	<i>R6</i>	$A \wedge B$	—	Circulate-left with <i>C</i>
1 1 1	<i>R7</i>	<i>R7</i>	<i>R7</i>	\bar{A}	—	—

Processor Unit

□ Examples of Micro-operations

Microoperation	Control word						Function
	<i>A</i>	<i>B</i>	<i>D</i>	<i>F</i>	<i>C_{in}</i>	<i>H</i>	
$R1 \leftarrow R1 - R2$	001	010	001	010	1	000	Subtract $R2$ from $R1$
$R3 \sim R4$	011	100	000	010	1	000	Compare $R3$ and $R4$
$R5 \leftarrow R4$	100	000	101	000	0	000	Transfer $R4$ to $R5$
$R6 \leftarrow \text{Input}$	000	000	110	000	0	000	Input data to $R6$
$\text{Output} \leftarrow R7$	111	000	000	000	0	000	Output data from $R7$
$R1 \leftarrow R1, C \leftarrow 0$	001	000	001	000	0	000	Clear carry bit C
$R3 \leftarrow \text{shl } R3$	011	011	011	100	0	010	Shift-left $R3$ with $I_L = 0$
$R1 \leftarrow \text{crc } R1$	001	001	001	100	0	101	Circulate-right $R1$ with carry
$R2 \leftarrow 0$	000	000	010	000	0	011	Clear $R2$

Processor Unit

❑ Other operations

- How to shift the contents of a specific register?
- **How to clear a specific register?**
 - There are several ways to perform these operations
 - We need to find the simplest one.


Lesson-16:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Design of Accumulator	<ul style="list-style-type: none">• To identify the requirements of accumulator design• To design an accumulator using JK flipflop.	Class Lecture Question and answer	Test, exams, quiz, etc

Design of Accumulator

□ Accumulator

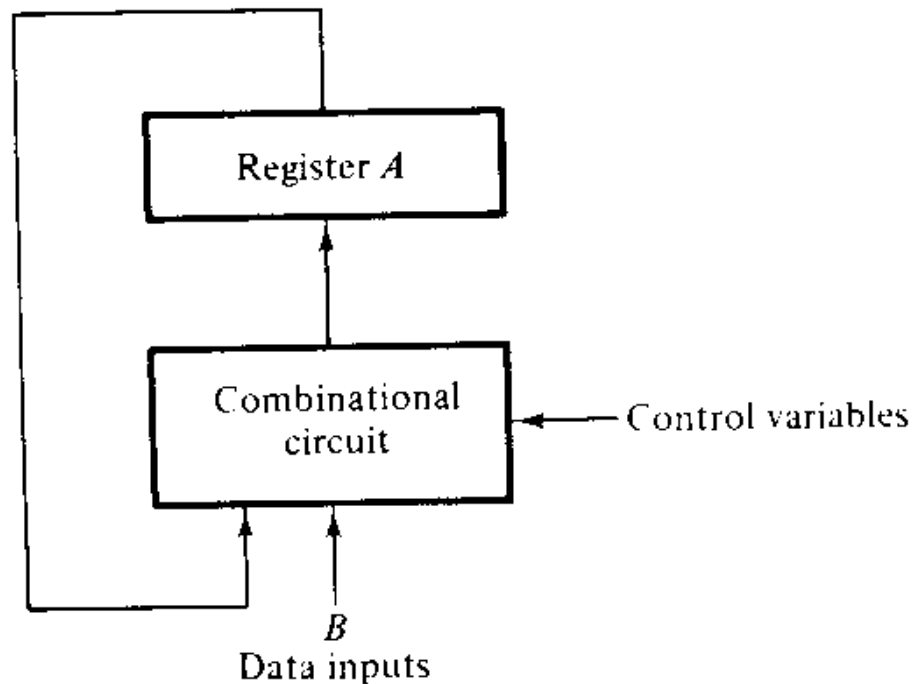- Not only the 'register A' but the combinational circuit is also a part of the accumulator.



Design of Accumulator

□ Accumulator

- A multi-functional register
 - **Not only perform the operations of commonly used register.**
 - **It should be perform all the micro-operations in a processor unit.**
 - **Also termed as multipurpose operational register.**
 - **The design of accumulator is dependent on the number of micro-operations it should be performed.**

Design of Accumulator

□ List of micro operations for an accumulator

Control variable	Microoperation	Name
p_1	$A \leftarrow A + B$	Add
p_2	$A \leftarrow 0$	Clear
p_3	$A \leftarrow \bar{A}$	Complement
p_4	$A \leftarrow A \wedge B$	AND
p_5	$A \leftarrow A \vee B$	OR
p_6	$A \leftarrow A \oplus B$	Exclusive-OR
p_7	$A \leftarrow \text{shr } A$	Shift-right
p_8	$A \leftarrow \text{shl } A$	Shift-left
p_9	$A \leftarrow A + 1$	Increment
	If ($A = 0$) then ($Z = 1$)	Check for zero

Design of Accumulator

□ Design procedure

- Each stage of the accumulator should be designed separately
 - Stages A_i should be connected in sequence $i=1, \dots, n$.
 - Each stage should be designed with a flip-flop
 - In this example we will use JK flip-flop,
 - Characteristics of JK flip-flop

$$Q(t + 1) = JQ' + KQ$$

- Control variables should be mutually exclusive.

Design of Accumulator

□ Design procedure

- Add **B** to **A**
- Control variable p_1

Present state	Inputs		Next state	Flip-flop inputs		Output
A_i	B_i	C_i	A_i	JA_i	KA_i	C_{i+1}
0	0	0	0	0	X	0
0	0	1	1	1	X	0
0	1	0	1	1	X	0
0	1	1	0	0	X	1
1	0	0	1	X	0	0
1	0	1	0	X	1	1
1	1	0	0	X	1	1
1	1	1	1	X	0	1

		B_i	
		1	1
A_i	X	X	X
	X	X	X
	X	X	X
	X	X	X
		C_i	

$$JA_i = B_i C_i' + B_i' C_i$$

X	X	X	X
	1		1

$$KA_i = B_i C_i' + B_i' C_i$$

		1	
	1	1	1

$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$

Design of Accumulator

□ Design procedure

- Add **B** to **A** (control variable p_1)
 - The Boolean function with control variable

$$JA_i = B_i C_i' p_1 + B_i' C_i p_1$$

$$KA_i = B_i C_i' p_1 + B_i' C_i p_1$$

$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$

Design of Accumulator

□ Design procedure

– Clear A (p_2)

- We need only apply control variable to K.

$$Q(t+1) = JQ + K'Q$$

- The Boolean function

$$JA_i = 0$$

$$KA_i = p_2$$

– Complement (p_3)

- The Boolean function

$$JA_i = p_3$$


$$KA_i = p_3$$

Design of Accumulator

□ Design procedure


– AND (p_4)

Present state	Input	Next state	Flip-flop inputs	
A_i	B_i	A_i	JA_i	KA_i
0	0	0	0	X
0	1	0	0	X
1	0	0	X	1
1	1	1	X	0

 

– OR (p_5)

Present state	Input	Next state	Flip-flop inputs	
A_i	B_i	A_i	JA_i	KA_i
0	0	0	0	X
0	1	1	1	X
1	0	1	X	0
1	1	1	X	0

 


Design of Accumulator

□ Design procedure

– XOR (p_6)

Present state	Input	Next state	Flip-flop inputs	
A_i	B_i	A_i	JA_i	KA_i
0	0	0	0	X
0	1	1	1	X
1	0	1	X	0
1	1	0	X	1

 

– Shift right (p_7) $JA_i = A_{i+1}p_7$

$$KA_i = A'_{i+1}p_7$$

– Shift left (p_8) $JA_i = A_{i-1}p_8$


$$KA_i = A'_{i-1}p_8$$

Design of Accumulator

□ Design procedure

– Increment (p_9)

 - Similar with synchronous counter of fig. 7-17




$$\begin{aligned}
 JA_i &= E_i \\
 KA_i &= E_i \\
 E_{i+1} &= E_i A_i \quad i = 1, 2, \dots, n \\
 E_1 &= p_9
 \end{aligned}$$

Design of Accumulator

□ Design procedure

- Check for zero (**Z**)

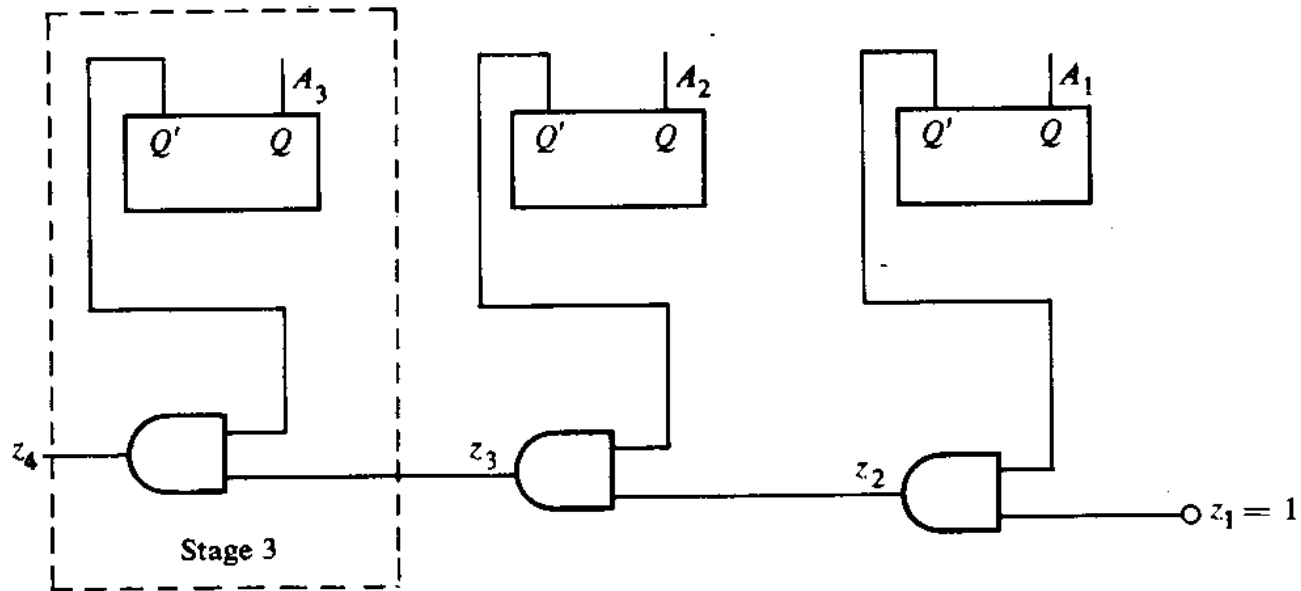

$$z_{i+1} = z_i A'_i \quad i = 1, 2, \dots, n$$

$$z_1 = 1$$

$$z_{n+1} = Z$$

Design of Accumulator

□ Design procedure

- One stage of accumulator

$$JA_i = B_i C'_i p_1 + B'_i C_i p_1 + p_3 + B_i p_5 + B_i p_6 + A_{i+1} p_7 + A_{i-1} p_8 + E_i$$

$$KA_i = B_i C'_i p_1 + B'_i C_i p_1 + p_2 + p_3 + B'_i p_4 + B_i p_6 + A'_{i+1} p_7 \\ + A'_{i-1} p_8 + E_i$$


$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$

$$E_{i+1} = E_i A_i$$

$$z_{i+1} = z_i A'_i$$

Design of Accumulator

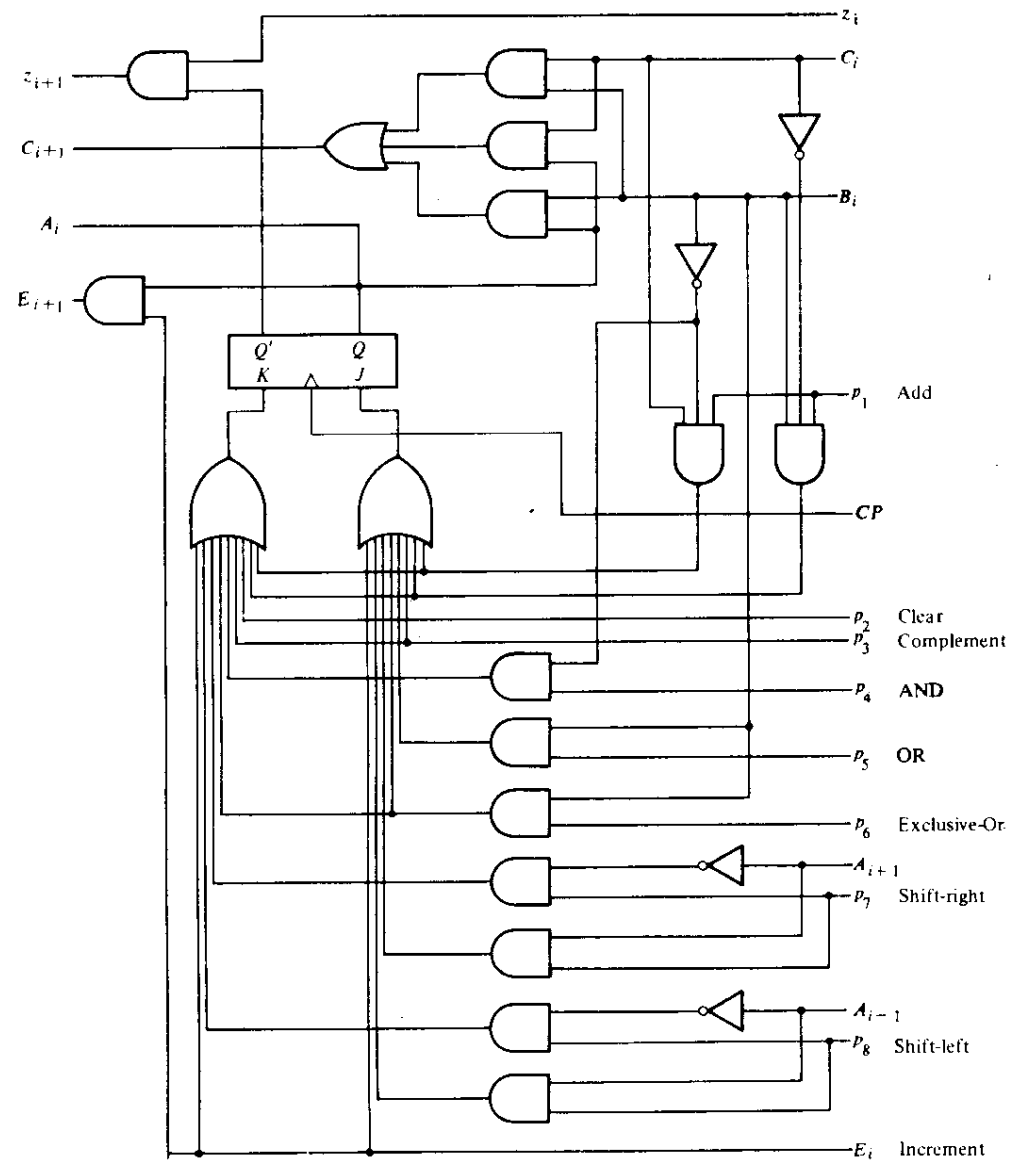
- Design procedure
 - One stage of accumulator



Design of Accumulator

□ Design procedure

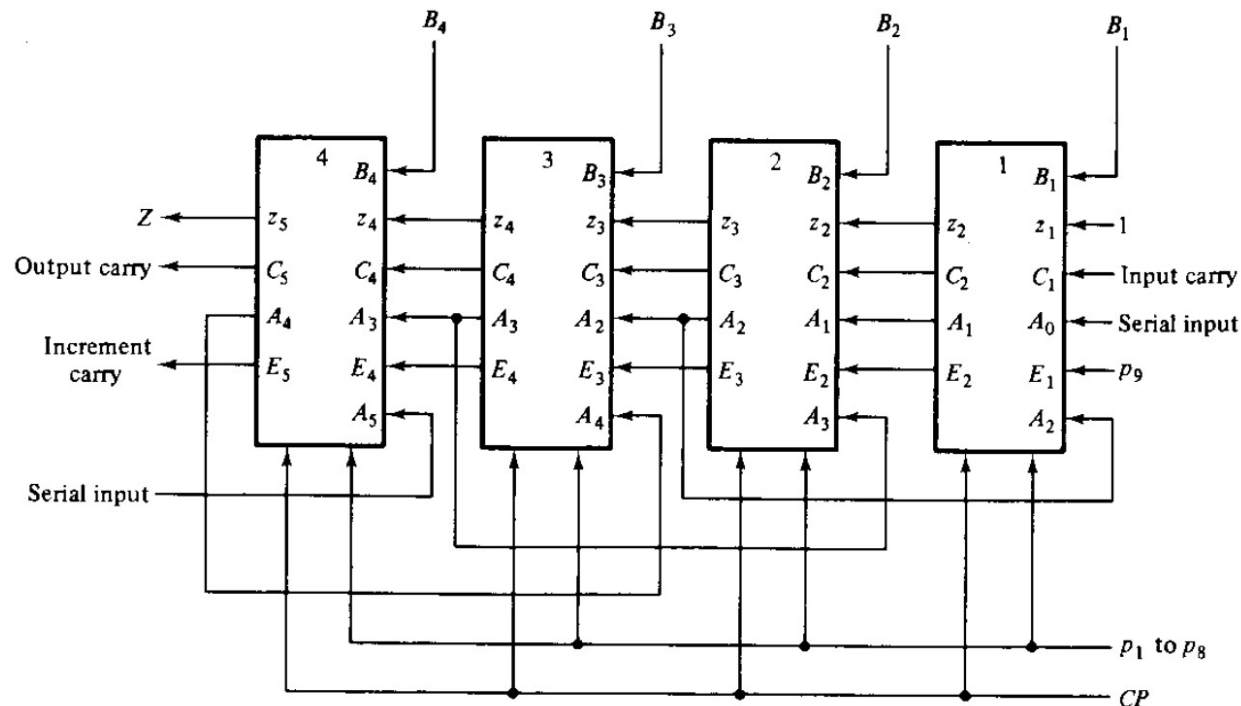- Complete accumulator
- 4-bit accumulator with 4 stages



Lesson-17:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Solving problems of Chapter-9	<ul style="list-style-type: none">To improve the problem solving skills	Class Lecture Homework	Test, exams, quiz, assignment, etc